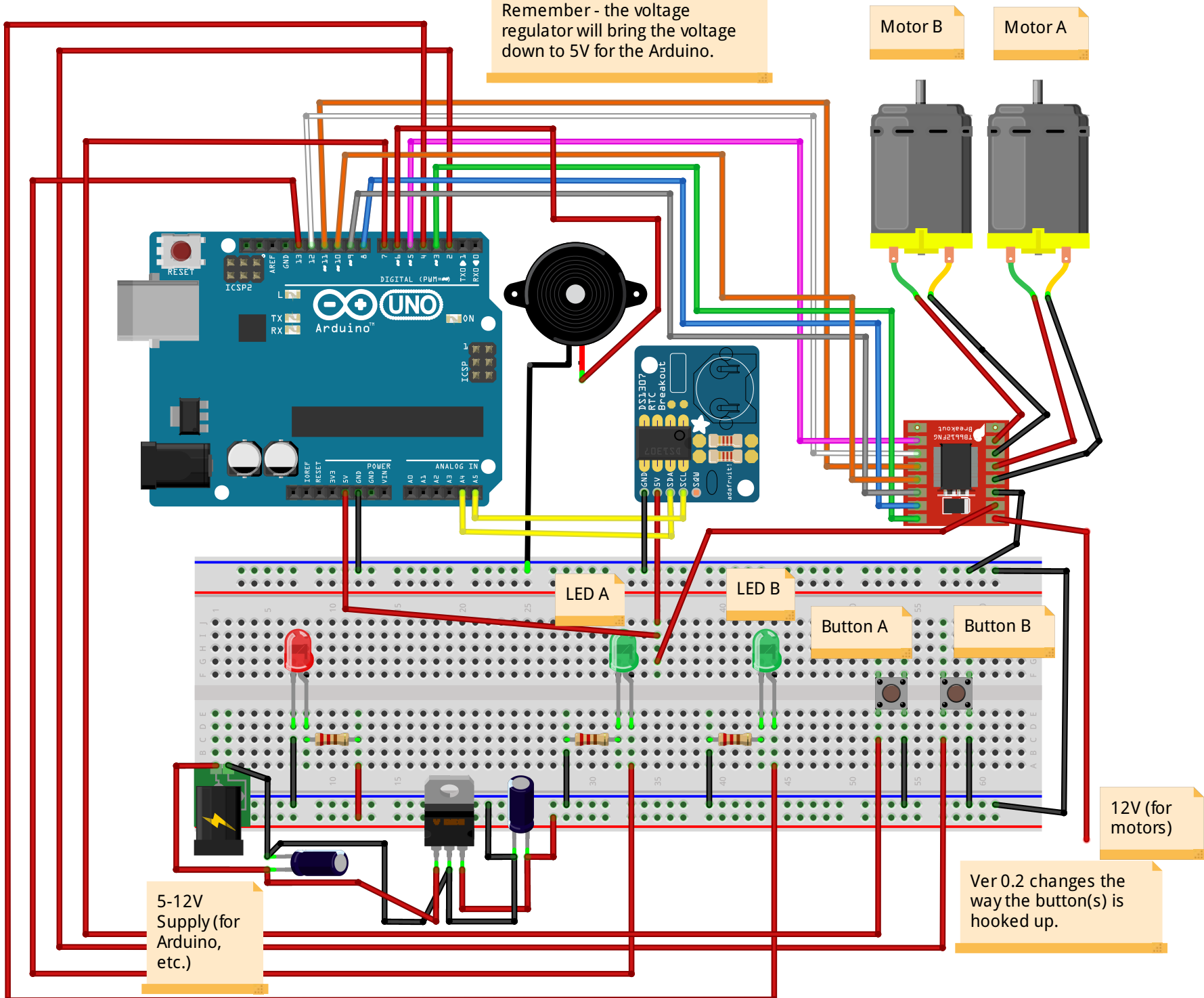


Note - you need 2 separate power supplies for this circuit - a 12V for the motors, and something like a 9V supply for the rest (Arduino, LEDs, Piezo, etc.)

Remember - the voltage regulator will bring the voltage down to 5V for the Arduino.



12V (for motors)

Ver 0.2 changes the way the button(s) is hooked up.